

Experiment No. - 05

Common Base (CB)

Object :-

Current Transfer characteristic of Common Base transfer configuration.

Apparatus required :-

NPN transistor kit, milliammeters, multimeter Voltmeter, power supply connection wires.

Formula use :-

$$\alpha_{ac} = \frac{\Delta I_c}{\Delta I_E} \checkmark$$

## Construction :-

### The Bipolar Junction Transistor :-

Basically, it consists of two back-to-back p-n Junction manufactured in a single piece of a semiconductor crystal. These two junctions give rise to three regions called emitter base and collector.

The emitter base and collector are provided with terminals which are labelled as E, B and C. The two junctions are: emitter-base (E/B) Junction and collector-base (C/B) junction. For NPN transistor it points from base to emitter meaning that base (and collector as well) is positive with respect to emitter.

#### 1. Emitter :-


It forms the left-hand section of region of the transistor as shown in fig.

It is more heavily doped than any of the other regions because its main function is to supply majority charge carriers to the base.


2. Base :-

It forms the middle section of the transistor. It is very thin ( $10^{-6}m$ ) as compared to either the emitter or collector and is very lightly doped.

(a)

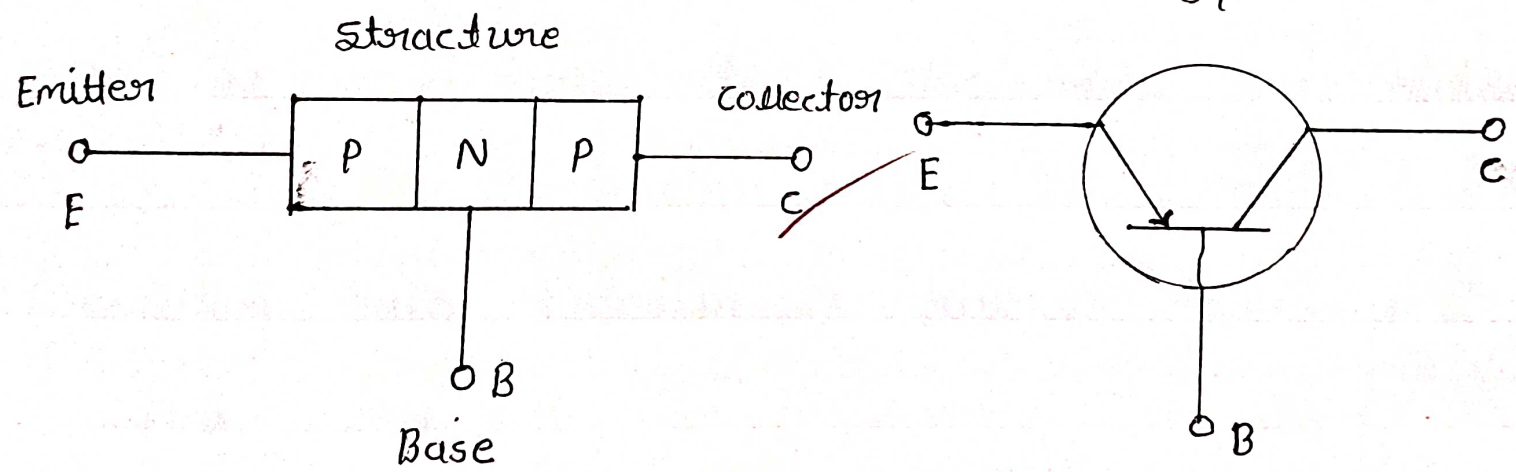

(b)

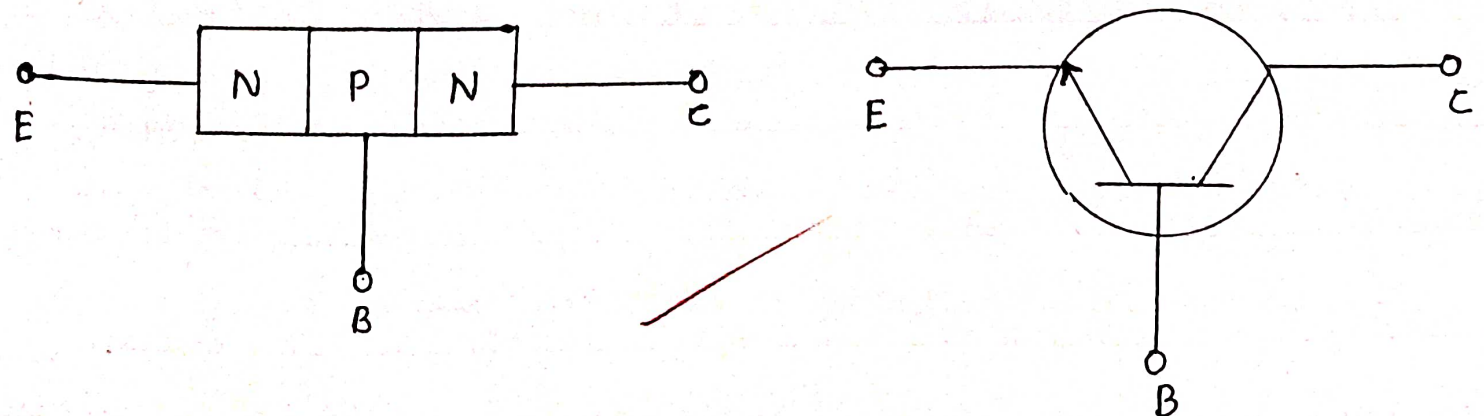





### 3. Collector :-

It forms the right-hand side section of the transistor shown in fig. and its main function is to collect majority charge carriers through the base.


### Transistor Biasing :-

For proper operation of a transistor it is essential to apply voltage of correct polarity across its two junctions. It is worthwhile to remember that the normal operation.

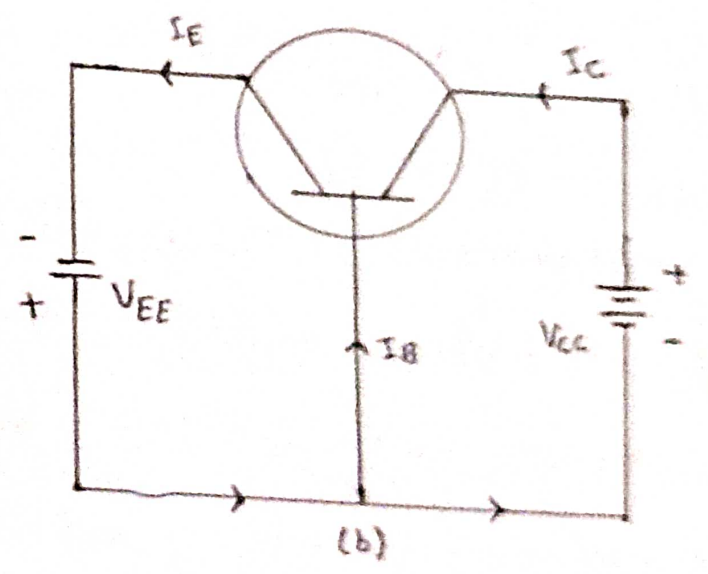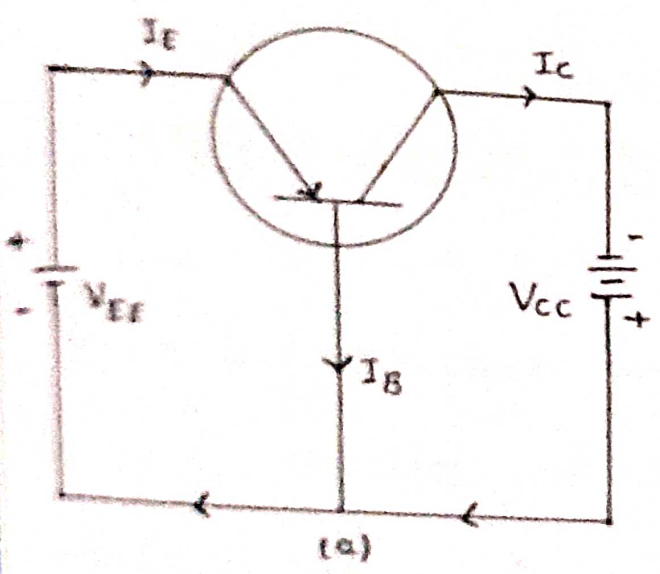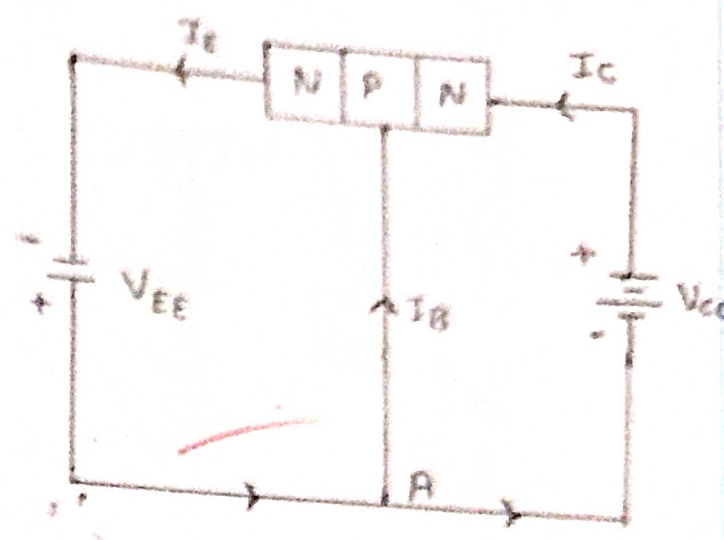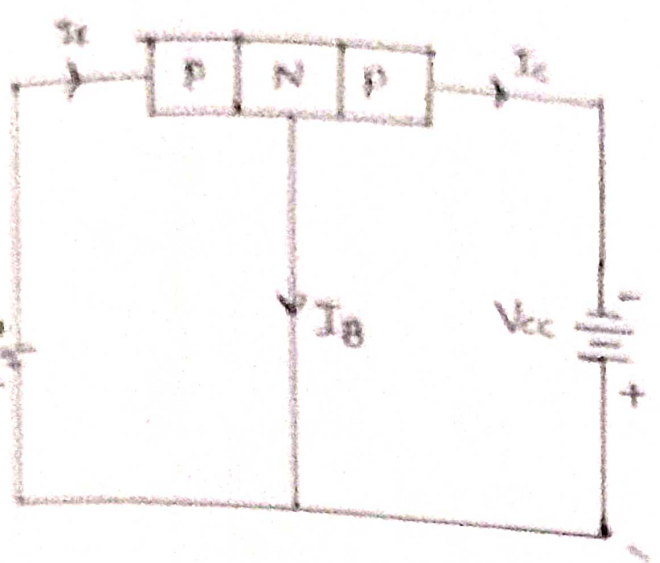
1. emitter - base junction is always forward biased, and
2. Collector - base junction is always reverse biased.



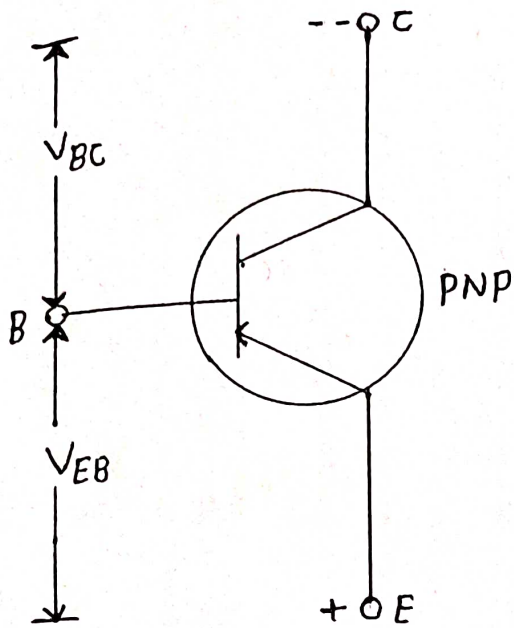In fig. two batteries respectively provide the dc emitter supply voltage  $V_{EE}$  and collector supply voltage  $V_{CC}$  for properly biasing the two junctions of the transistor.




(a)

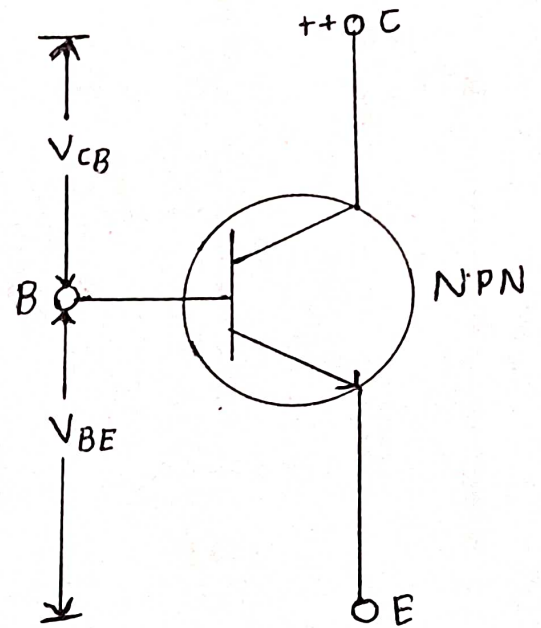

(b)
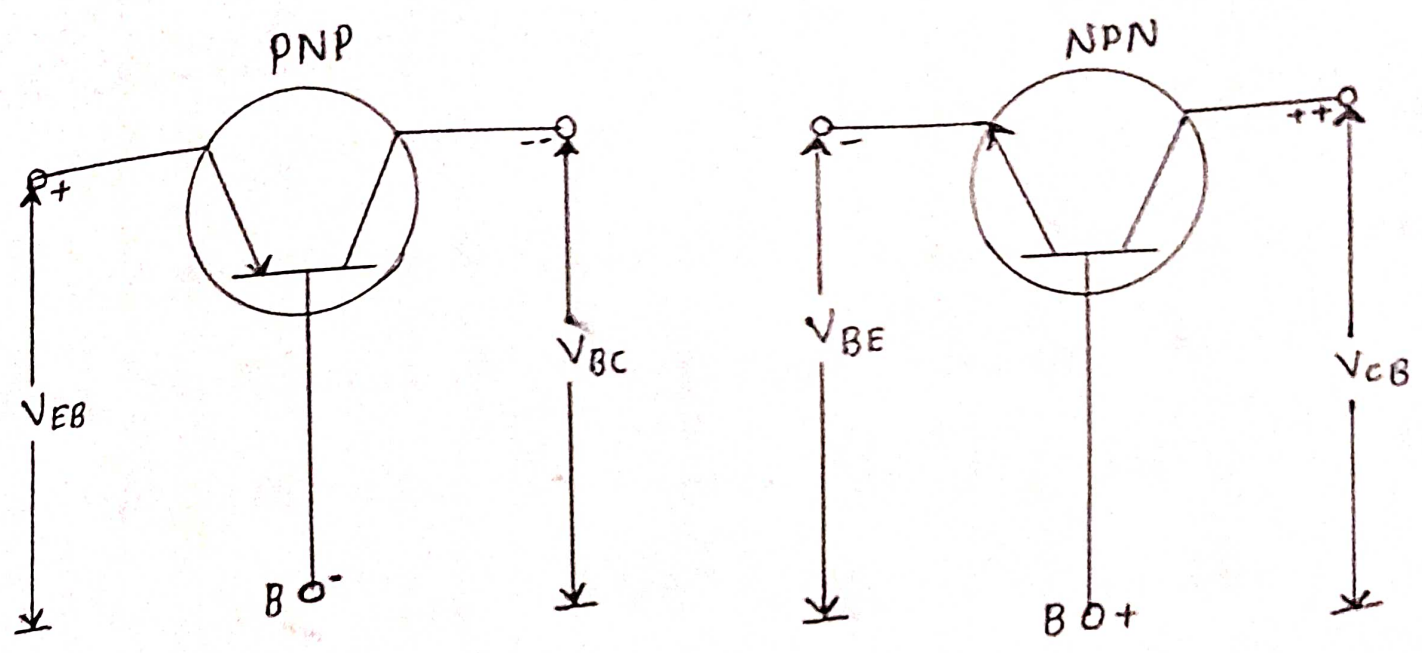
### Important Biasing Rule :-


For a PNP transistor both collector and base are negative with respect to the emitter of course, collector is more negative than base. Similarly for NPN transistor both collector and base are positive with respect to the emitter. A gain collector is more positive than the base as shown in fig.



respect to base. Now between the base and collector themselves, collector is ~~is~~ more negative than base. Hence their potential difference is written as  $V_{BC}$  and note as  $V_{CB}$  Same is the case with voltage marked in fig.
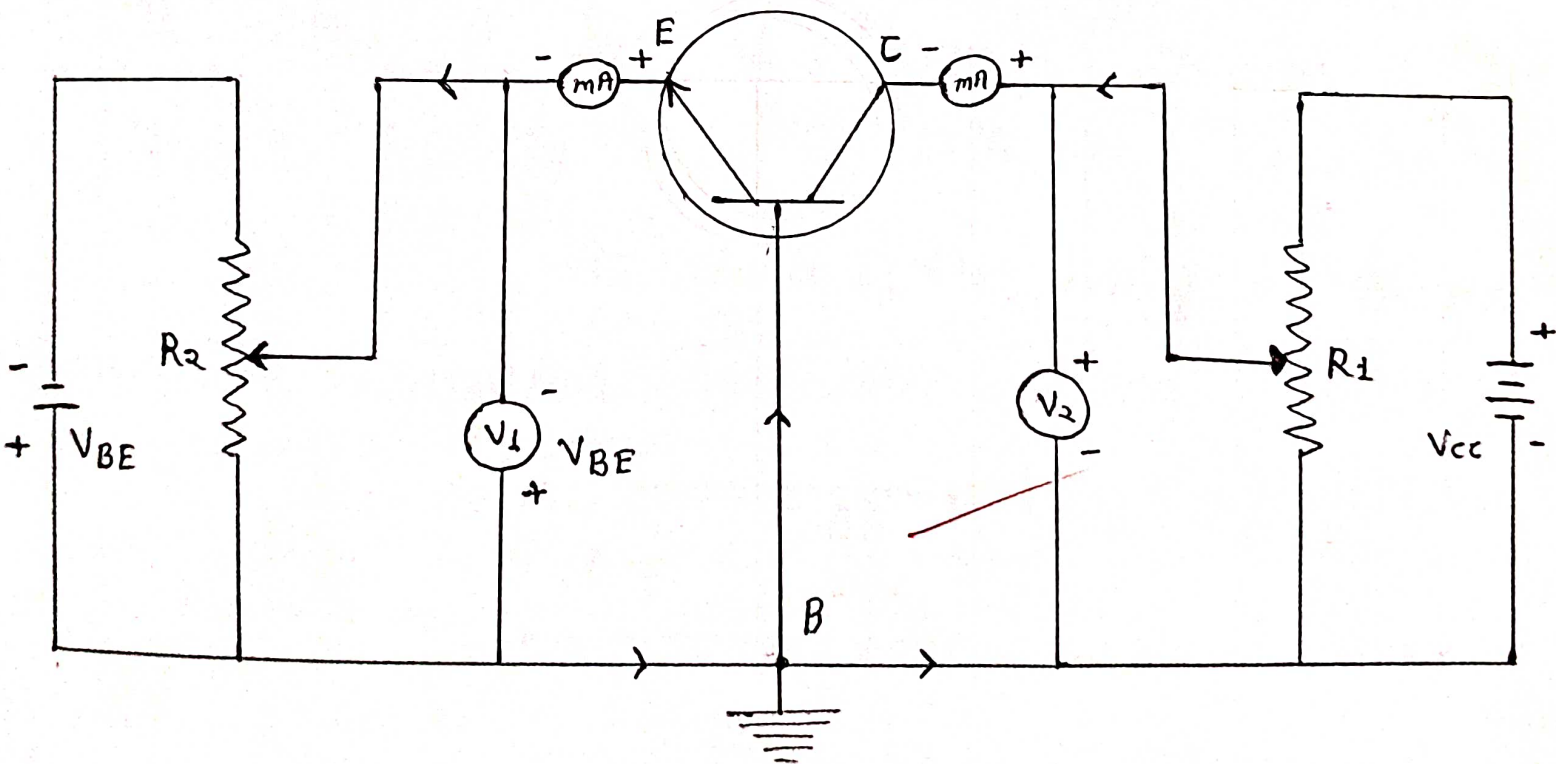
## Common Base Test Circuit :-

The static characteristics of an NPN transistor connected in common-base configuration can be determined by the use of test circuit shown in fig. millimeters are included in series with the emitter and collector circuits to measure  $I_E$  and  $I_C$  similarly voltmeters are connected



Circuit :- NPN Transistor in CB mode



across E and B to measure Voltage  $V_{BE}$  and  
across C and B to measure  $V_{CB}^*$

### Current Transfer Characteristic :-

It shows how  $I_c$  varies with changes in  $I_E$  when  $V_{CB}$  is held constant. For drawing this characteristic first  $V_{CB}$  is set a convenient value and the  $I_E$  is increased in steps and corresponding values of  $I_c$  noted. A typical transfer characteristic is shown in fig.

As seen,  $\alpha_{ac}$  may be found from the equation.

$$\alpha_{ac} = \frac{\Delta I_c}{\Delta I_E}$$

usually  $\alpha_{ac}$  is found from output characteristic than from this characteristic.

It may be noted in the end that CB Connection is scarcely employed for audio - frequency circuits because (i) its current gain is less than unity and (ii) Its input and output resistances are so different.


Observation table :-

S.N.	Input emitter current $I_E$ in (mA)	output collector current $I_C$ in (mA)
1.	0	0
2.	5	5
3.	10	9
4.	15	16
5.	20	21
6.	25	26
7.	30	31
8.	35	35
9.	40	40
10.		

Scale

on x axis as small div = 1 unit

on y axis as small div = 5 unit

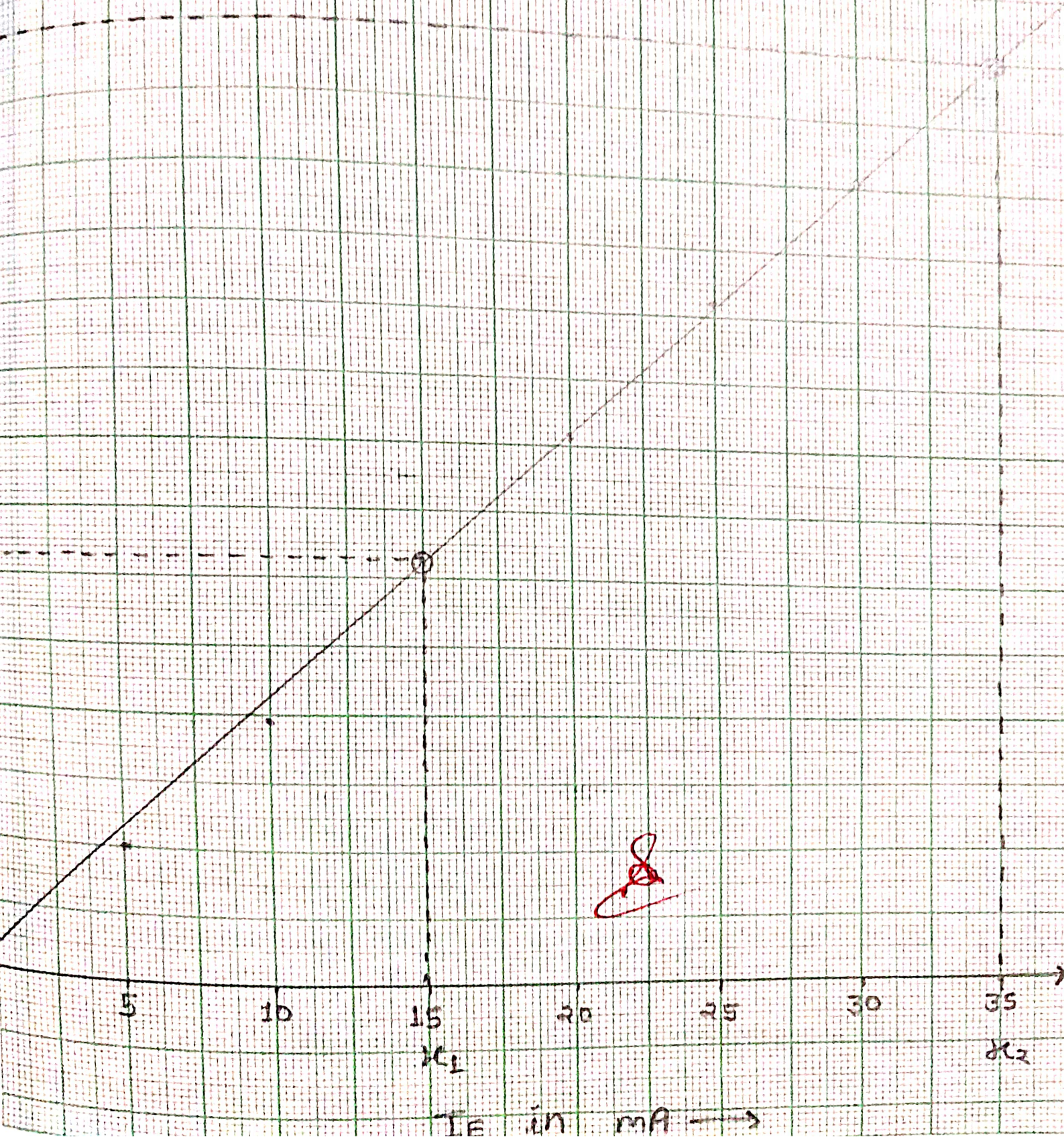

Calculation :-

$$\Delta I_c = 35 - 16 \quad \text{and} \quad \Delta I_E = 35 - 15$$

$$\Delta I_c = 19$$

$$\Delta I_E = 20$$

then,

$$\alpha_{ac} = \frac{\Delta I_c}{\Delta I_E}$$

$$\alpha = \frac{19}{20}$$

$$\alpha = 0.95$$

$$\alpha = 0.95 < 1$$

Result :-

The current gain of this given NPN transistor in common-base configuration is  $\alpha = 0.95$

*Seen/checked by*  
*6/1/23*