

**Object :** *To study the characteristic curve of solar cell.*

**Apparatus Required :** Solar cell, millivoltmeter, micrometer and variable load.

**Theory :** A solar cell is the photo-voltaic device which converts the solar energy radiations directly into the electrical energy with an efficiency of the order of 10%. It is basically a P-N junction with a large surface area which operates at the zero bias voltage.

When solar radiations fall at the junction, electron-hole pair are formed in both sides of junction due to breaking of covalent bonds.

Now due to accumulation of holes in P region and electrons in N region, a voltage is developed across the junction which makes the P-N junction in forward bias condition. As a result, a current  $I$  begins to flow from P region to N region, through the junction. When no load is connected in the circuit, the forward current  $I$  balances the current  $I_g$  due to sweep of electrons and holes at the junction. But when an external load  $R_L$  is connected between P and N sides of solar cell, a current  $I_L$  begins to flow through the load which develops a potential difference  $V_L$  across the load and thus light (or solar) energy is converted into the electrical energy.

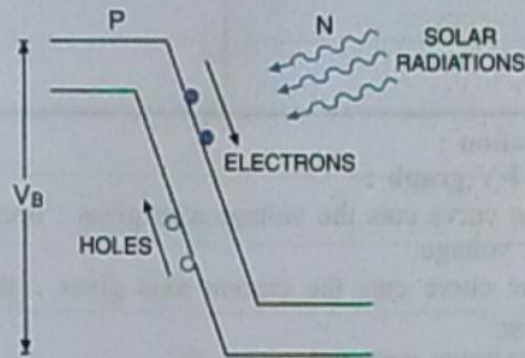


Fig. 63. Absorption of solar radiation

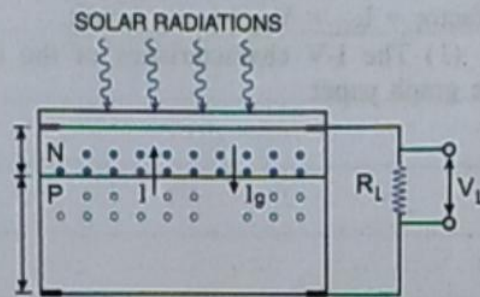


Fig. 64. P-N junction after being illuminated with solar radiations

Procedure : (1) The circuit is connected as shown in Fig. 64.

(2) Note down the voltage at maximum load *i.e.*, when current = 0. This gives the open circuit voltage  $V_{OC}$ .

(3) The load is reduced in steps and corresponding voltage and current are noted down. Take 8-10 readings.

(4) Minimise the load and note down the short circuit current  $I_{SC}$  *i.e.*, the current when  $V = 0$ .

(5) A graph for current versus voltage is drawn (Fig. 65)

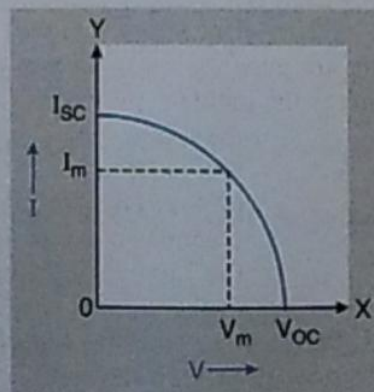


Fig. 65. I-V graph of solar cell

(6) Find  $I_m$ ,  $V_m$ ,  $I_{SC}$  and  $V_{OC}$  from I-V graph.

(7) Calculate fill factor for a given solar cell.

### Observations :

S.No.	Voltage across solar cell (in volt)	Current in the circuit (in $\mu\text{A}$ )
1.		
2.		
3.		
4.		
5.		
6.		
7.		
8.		
9.		
10.		

### Calculation :

#### From I-V graph :

(1) The curve cuts the voltage axis gives : open circuit =  $V_{oC} = \dots\dots$  voltage.

(2) The curve cuts the current axis gives : short circuit current =  $I_{SC}$

(3) Maximum current  $I_m = \dots\dots$  A

(4) Maximum voltage  $V_m = \dots\dots$  volt

(5) Fill factor =  $I_{SC} \times V_{oC} = \dots\dots$  A volt.

**Result :** (1) The I-V characteristics of the solar cell is shown on the graph paper.

(2) The efficiency of a given solar cell  $\eta = \dots\dots\dots$  %.

(3) Fill factor of given solar cell =  $\dots\dots\dots$  .

**Precautions :** (1) The positive terminal of solar cell should be connected to positive terminals of voltmeter and ammeter.

(2) After doing experiment switch off the circuit.